

PRN No.	Total No. of Questions: 09
---------	----------------------------

QP Code:

EIEFY 25524 (8)
23-24

JSPM's

Rajarshi Shahu College of Engineering, Tathawade, Pune- 411033

(An autonomous institute affiliated to Savitribai Phule Pune University)

Examination: End Semester Examinations (ESE)

Semester: II

Academic Year: 2023-24

Class: F. Y. B. Tech.

Department: Engineering Sciences and Humanities


Subject Code: EC1201- Subject Name and pattern: Basic Electronics Engineering (2023)

Duration: 2hrs

Max. Marks: 35 Mar

Instructions to the Candidates	
1.	In Section A, Q.1, Q. 2 and Q.3 are compulsory.
2.	In section B, Solve Q.4 or Q.5, Q.6 or Q.7 and Q.8 or Q.9.
3.	Assume suitable and necessary data wherever required.

Q. No.	Section-A	Marks	BL	CO
Q.1	Solve any One			
a	Compare the performance of HWR and FWR with respect to following parameters: i) Ripple Factor ii) VLDC iii) TUF	3	BL2	CO1
b	Find the current through the Zener diode when $E_i = 25V, V_Z = 5V$			

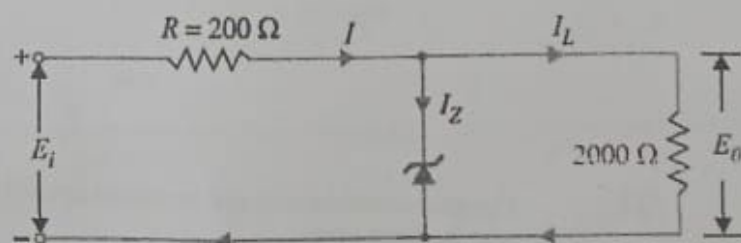


3 BL3 CO1

Q.2	Solve any One			
a	State the biasing conditions required for the three regions of operation of BJT	3	BL2	CO2

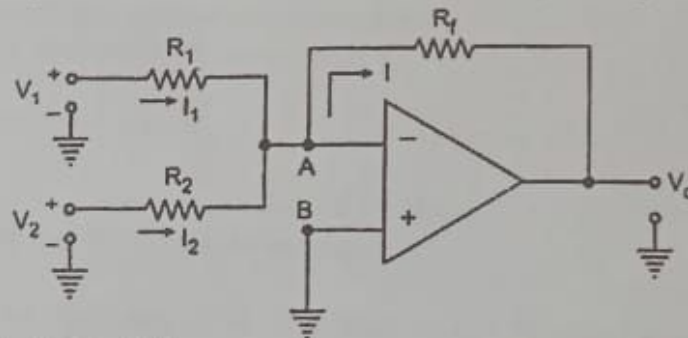- Q.3 b Explain single stage RC coupled CE amplifier with neat circuit diagram
Solve any One

3 BL2 CO2

- a Identify the circuit and derive an expression for Output voltage.




3 BL3 CO3

- b In Astable Multivibrator calculate Total Time and frequency if $R_A=10K\Omega$, $R_B=50K\Omega$ and $C=0.1\mu F$.

3 BL3 CO3

Section B

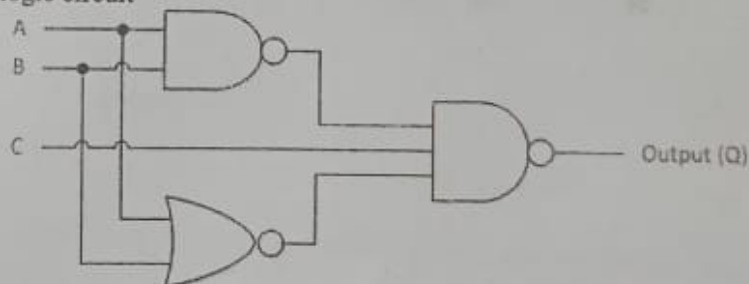- Q.4 a Identify the gates and Obtain the Boolean equation for the following logic circuit



5 BL3 CO4


- b What is Multiplexer? What is relation between number of inputs and select lines? Elaborate 4:1 MUX with Truth table

4 BL2 CO4

OR

- Q.5 a Compare combinational and sequential circuit? Explain SR Flip flop with its Truth table

5 BL2 CO4

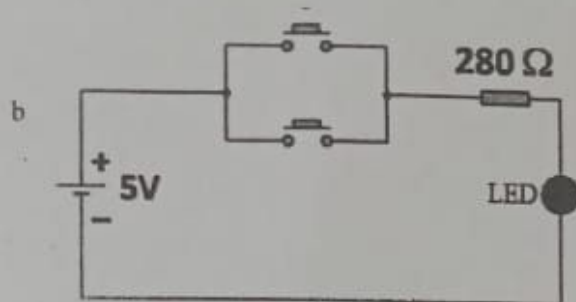

4 BL3 CO4

Identify the Gate and write its truth table .Which IC is used to perform the above function?

- Q.6 a Define dark current? Draw and explain the characteristics of phototransistor. 5 BL2 CO5
- b Which sensor is used in Security systems? Explain it with block diagram? 4 BL2 CO5

OR

- Q.7 a Elaborate the construction and working of LVDT with its advantages. 5 BL2 CO5
- b Which sensor is used in Agricultural field? Explain it with block diagram. 4 BL2 CO5
- Q.8 a Elaborate GSM with its block diagram? 4 BL2 CO5
- b Compare the performance of Amplitude and Frequency modulation.(at least 4 points) 4 BL3 CO6

OR

- Q.9 a A carrier of 25V peak and frequency 10MHz is amplitude modulated by a sine wave of 5V peak and Frequency 2000Hz.Determine the modulation index. Draw frequency spectrum for AM wave. 4 BL3 CO6
- b Draw the Amplitude modulation waveform for:
- Linear modulation
 - Over modulation
 - Under modulation
 - No modulation
- 4 BL2 CO6

*****BEST of LUCK*****