

PRN No. RB12817006	Total number of questions-6
-----------------------	--------------------------------

QP Code:

JSPM's
RajarshiShahu College of Engineering, Tathawade, Pune- 411033
(An autonomous institute affiliated to SavitribaiPhule Pune University)
Examination: Mid Semester Examinations (MSE)
Semester: II Academic Year: 2023-24

Class: F. Y. B. Tech. (All Programs)
Department: Engineering Sciences and Humanities

Subject Code: EC1201 Subject Name and pattern: Basic ElectronicsEngineering(2023)


Duration: 1 Hour

Max. Marks: 20 Marks

Instructions to the Candidates

1. Solve Q.1 or 2, Q.3 or 4, Q.5 or 6
2. Assume suitable and necessary data wherever required.
3. Neat diagram must be drawn wherever necessary

Q. No.		Marks	BL	CO
Q.1	a	03	BL3	CO1
	b	02	BL1	CO1

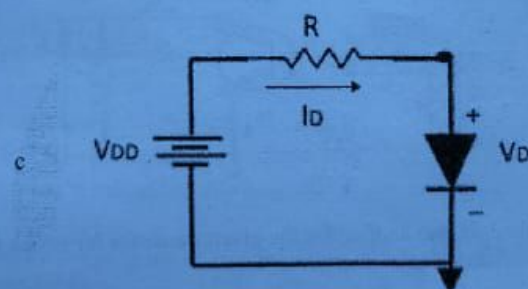

02 BL3 CO1

In the above circuit $V_{DD}=10V$, $R=920\Omega$ find the current through the circuit?

OR


Q.2 a From the following circuit answer the following questions---

1) What type of circuit it is?

2) Sketch the voltage waveform across R_L

3) calculate PIV if $V_{pri}=230V$, $V_{sec}(rms)=120V$, $R_L=1K\Omega$

03 BL3 CO1

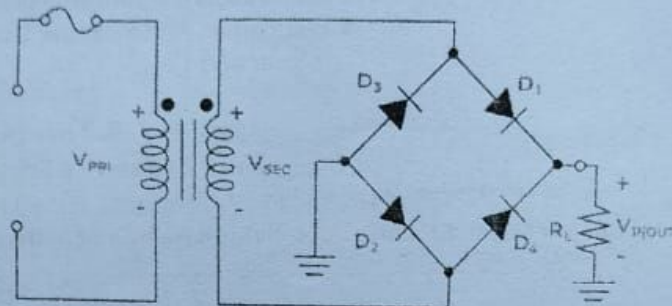

b A 50 V peak full wave rectified voltage is applied to a capacitor input filter. If $f=120Hz$, $R_L=100K\Omega$ and $C=1\mu F$ Determine the ripple factor?


02 BL3 CO1

c For zener voltage regulator if $I_Z(min)=2mA$, $I_Z(max)=20mA$, $V_Z=5V$. Determine the range of input voltage over which output voltage remains constant. $R_S=1K$, $R_L=1K$

02 BL3 CO1

Q.3 a Identify the circuit and draw its Input characteristics

02 BL3 CO2

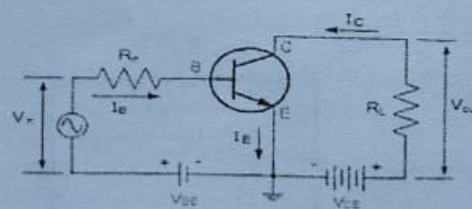

b Calculate α_{DC} and β_{DC} for the given transistor for which $I_C=10mA$; $I_B=85\mu A$

02 BL3 CO2

c What is current gain? Derive an expression for current gain in Common base and common Emitter configuration


02 BL2 CO2

Q.4 a Compare CB, CE and CC configuration on the basis of current gain, phase difference, input and output resistance

02 BL2 CO2

- b Determine I_B and I_C through the following circuit if $V_{CE}=0.1\text{ V}$
 $R_B=5\text{K}\Omega$, $R_C=500\Omega$, $V_{BB}=10\text{V}$, $V_{CC}=20\text{V}$

02 BL3 CO2

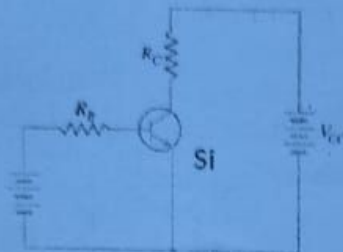


- c i) What are the biasing conditions of the base emitter and base collector junctions for a transistor to operate as a switch
 ii) What is Current equation for npn and pnp Transistor

02 BL1 CO2

Q.5

a

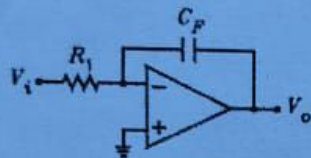

03 BL3 CO3

Identify the circuit and write the output equation

- b Explain the following parameters of an op amp and write the typical values for IC 741
 i) Slew Rate ii) Input resistance

02 BL2 CO3

- c IC 555 configured to run in astable mode with $R_1=2\text{K}\Omega$, $R_2=5\text{K}\Omega$ and $C=0.01\text{ }\mu\text{F}$. Determine the frequency of the output and duty cycle.

02 BL1 CO3

OR

- Q.6 a Elaborate the modes of operations of operational Amplifier

03 BL2 CO3

- b For the inverting amplifier using op-amp if $R_f=100\text{k}\Omega$, $R_1=10\text{k}\Omega$, $V_{cc}=12\text{V}$ calculate the output voltage if $V_i=4\text{V}$. Is the result practically possible?

02 BL3 CO3

- c Draw the circuit diagram of Non inverting summer and write the output equation

02 BL2 CO3

*****BEST of LUCK*****